

Year 6: Electricity

Key Learning

Symbols for different components in a circuit:



Battery



Wire




Bulb



Buzzer



Motor

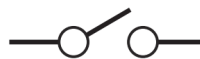

Open switch



Closed switch

More batteries or a higher voltage create more power to flow through the circuit.


By changing the components in a circuit we can vary:



The brightness of a bulb (brighter or dimmer)



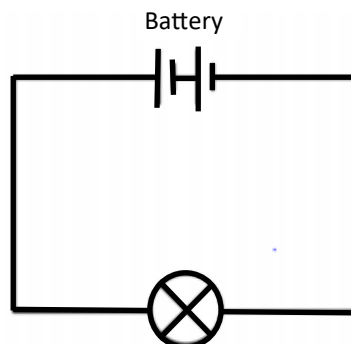The volume of a buzzer (louder or quieter)



Wir

- If you make the wires longer, the bulb will get dimmer. This is because there is more resistance.
- If you add more bulbs, the bulbs get dimmer. This is because there is also more resistance.
- If you add more batteries, the bulbs will get brighter. This is because there is less resistance and a greater current.

If a switch is open, the circuit is not complete. When a circuit is not complete, components such as bulbs, buzzers and motors will not work.



The hazard symbol warns of high voltage. You should not touch anything with this symbol on.

Key Vocabulary

current	A flow of electrons in a circuit
electrons	Very small particles that travel around an electric circuit and carry energy.
voltage	The force of an electrical current that makes electricity move through a wire.
battery	A container or one or more cells that is used to generate a current.
switch	A device used for making and breaking the connection in an electrical circuit.
filament	A conducting wire or thread with a high melting point which forms part of an electrical bulb.
static electricity	A stationary electric charge, typically produced by friction, which causes sparks, crackling or the attraction of dust.
resistance	A measure of the difficulty of passing an electric current through a conductor. The more resistance in a circuit, the less electricity will flow through.